


Programmable Processors

Course Project B




- Programmable processors
also named: 'stored program' processors
- Different tasks can be performed by
changing the program.
- Well-known examples: MIPS, ARM,
Pentium, PIC, Atmel, AtMega

Programmable Processors

State Machine

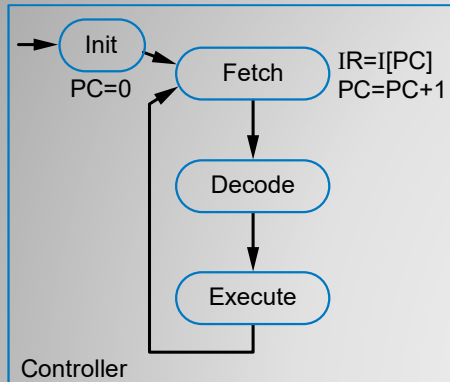


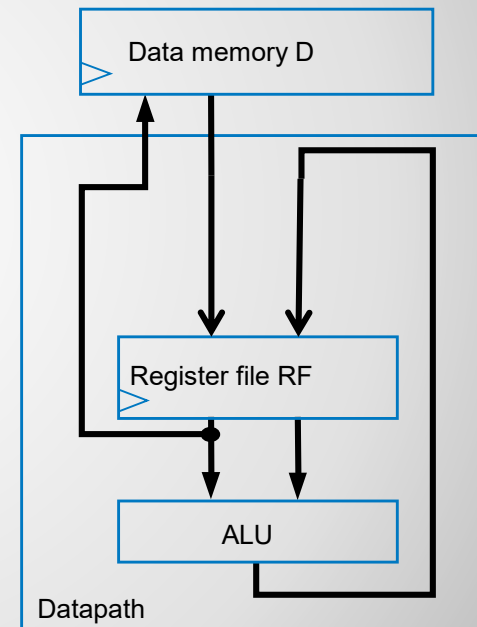  RF = Register File
D = Data Memory
I = Instruction Memory



From F. Vahid's *Digital Design*


Basic Architecture

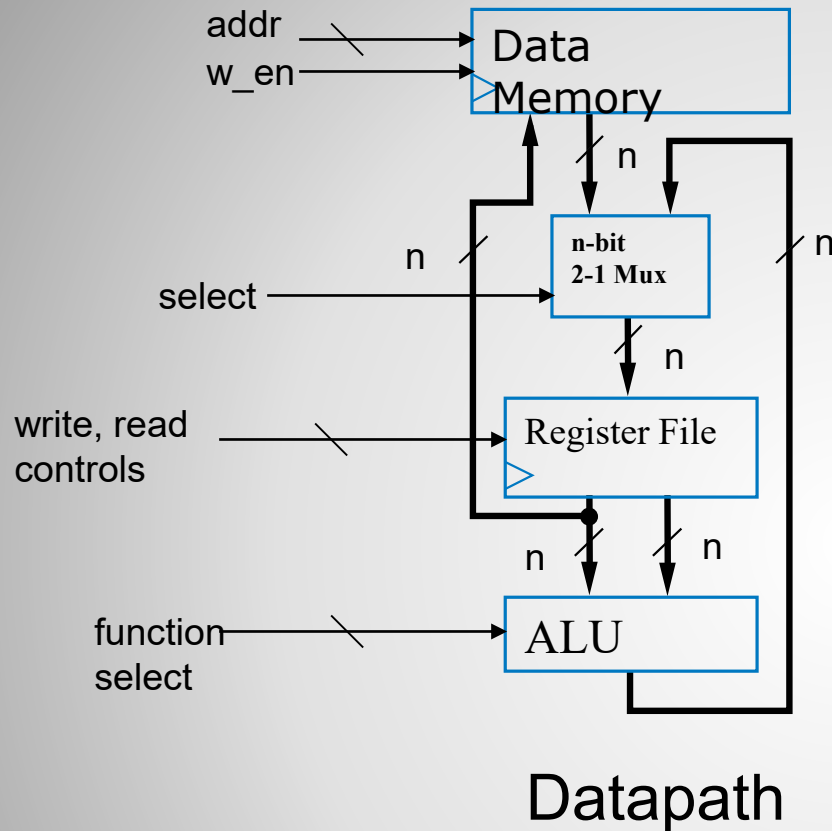


- Takes data from Data Memory
- Stores it in Register File
- Operates on it in ALU (puts it back into the Register File)
- Can store Register File data back into Data Memory
- Note the dual output Register File

Basic Architecture - Datapath


From F. Vahid's *Digital Design*

 

LOAD operation

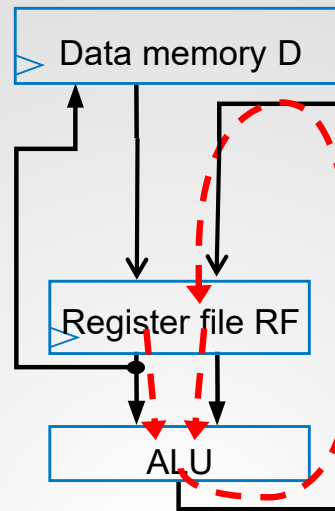

ALU operation
(like an ADD)

 

STORE operation

$D[9] = D[0] + D[1]$ – requires a sequence of four datapath operations:

LOAD 0: $RF[0] = D[0]$
 LOAD 1: $RF[1] = D[1]$
 ADD 2: $RF[2] = RF[0] + RF[1]$
 STORE3: $D[9] = RF[2]$


Each line here represents one instruction; so it takes four instructions to do this add

From F. Vahid's *Digital Design*

Basic Datapath Operations

- $D[9] = D[0] + D[1]$ – requires a sequence of four datapath operations:
 - 0: $RF[0] = D[0]$
 - 1: $RF[1] = D[1]$
 - 2: $RF[2] = RF[0] + RF[1]$
 - 3: $D[9] = RF[2]$
- Each operation is an *instruction*
 - Sequence of instructions = *program*
 - Looks cumbersome, but that's the world of programmable processors – Decomposing desired computations into processor-supported operations
 - Store program in *Instruction memory*
 - *Control unit* reads each instruction and executes it on the datapath
 - PC: Program counter – address of current instruction
 - IR: Instruction register – current instruction

RF = Register File
D = Data Memory

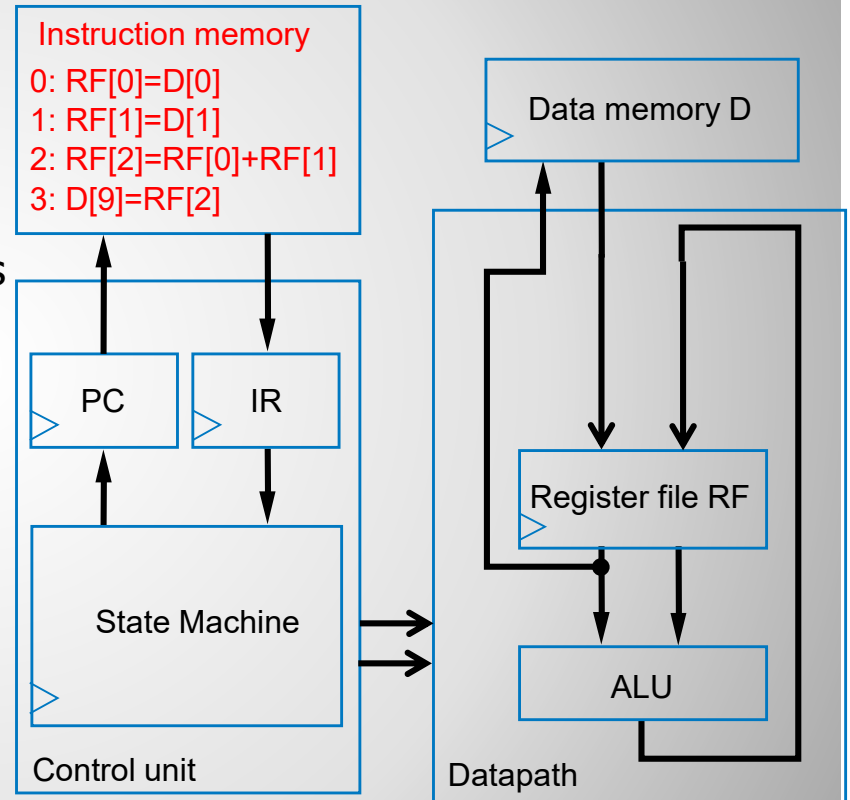

Basic Architecture – Control


From F. Vahid's *Digital Design*

We will take

- Data memory (RAM): 256 X 16
- Instruction memory (ROM): 128 X 16
- Register file: 16 X 16
- ALU: Two 16-bit inputs, 16-bit output


The Sizes of Things

State Machine

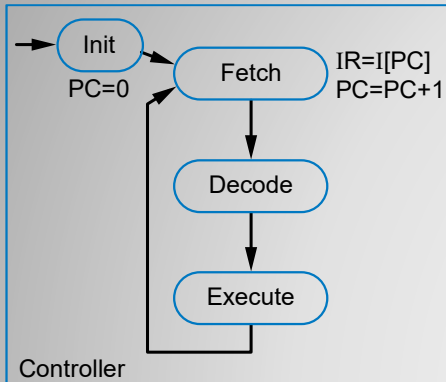

To summarize, the control unit processes each instruction in three stages:

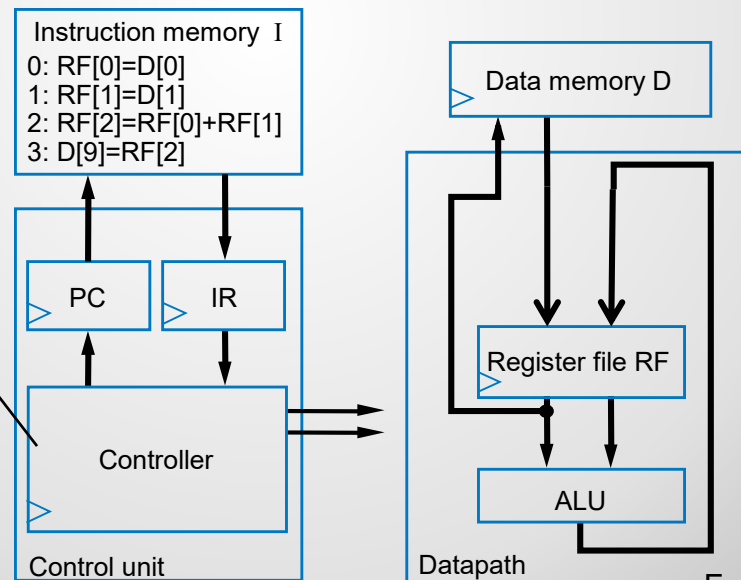1. first *fetching* the instruction by loading the current instruction into *IR* and incrementing the *PC* for the next fetch,
2. next *decoding* the instruction to determine its operation, and
3. finally *executing* the operation by setting the appropriate control lines for the datapath, if applicable. If the operation is a datapath operation, the operation may be one of three possible types:
 - (a) *loading* a data memory location into a register file location,
 - (b) transforming data using an *ALU* operation on register file locations and writing results back to a register file location, or
 - (c) *storing* a register file location into a data memory location.



From F. Vahid's *Digital Design*

Basic Architecture – Control

- Instruction Set – List of allowable instructions and their representation in memory
- Each of our instructions is 16 bits long
- Most of them contain some address information
- General form : **operation source destination**

NOOP instruction – **0000 0000 0000 0000**

STORE instruction – **0001** $r_3r_2r_1r_0$ $d_7d_6d_5d_4d_3d_2d_1d_0$

LOAD instruction – **0010** $d_7d_6d_5d_4d_3d_2d_1d_0$ $r_3r_2r_1r_0$

ADD instruction – **0011** $ra_3ra_2ra_1ra_0$ $rb_3rb_2rb_1rb_0$ $rc_3rc_2rc_1rc_0$

SUBTRACT instruction – **0100** $ra_3ra_2ra_1ra_0$ $rb_3rb_2rb_1rb_0$ $rc_3rc_2rc_1rc_0$

HALT instruction – **0101 0000 0000 0000**

`r's are Register File locations (4 bits each)
 `d's are Data Memory locations (8 bits each)

Data memory (RAM):
 256 X 16

Register file: 16 X 16

Six-Instruction Processor

- **0000 0000 00000000**
- Always starts with **0000** (and contains nothing but zeros)
- Actually is just 0000 xxxx xxxxxxxx, since the 12 bits following 0000 are ignored.
- NoOp = No Operation
- Just takes up space (or time)
- Does not involve the Datapath
- If your program starts executing a string of 0s, nothing (too) bad will happen.

NOOP Instruction

- **0001 r₃r₂r₁r₀ d₇d₆d₅d₄d₃d₂d₁d₀**
- Always starts with **0001**
- **r₃r₂r₁r₀** is a 4-bit Register File address (source)
- **d₇d₆d₅d₄d₃d₂d₁d₀** is a Data Memory address (destination)
- Moves 16 bits of data from the Register File to Data Memory
- Example: 0001 1111 0010 1001b (or 0x1F29) means "move the data at Register File 0xF (15d) to Data Memory location 0x29 (41d)"

STORE Instruction

- **0010 d₇d₆d₅d₄d₃d₂d₁d₀ r₃r₂r₁r₀**
- Always starts **0010**
- **d₇d₆d₅d₄d₃d₂d₁d₀** is a Data Memory address (source) – here d implies D memory
- **r₃r₂r₁r₀** is a 4-bit Register File address (destination)
- Moves 16 bits of data from Data Memory to the Register File
- Example : 0010 00001010 0111b (or 0x20A7) means “move the data at Data Memory location 0x0A (10d) to Register File 7.”

LOAD Instruction

- **0011 ra₃ra₂ra₁ra₀ rb₃rb₂rb₁rb₀ rc₃rc₂rc₁rc₀**
- Always starts with **0011**
- **ra₃ra₂ra₁ra₀** is a 4-bit Register File address (source for A)
- **rb₃rb₂rb₁rb₀** is a 4-bit Register File address (source for B)
- **rc₃rc₂rc₁rc₀** is a 4-bit Register File address (destination)
- Adds the 16 bits of A to 16 bits of B, stores the result in C (all these in the Register File)
- Example: 0011 0001 0010 0011b
(or 0x3123) adds the data at Register File 1 to the data at Register File 2 and stores the result in Register File 3.

ADD Instruction

- **0100** **ra₃ra₂ra₁ra₀** **rb₃rb₂rb₁rb₀** **rc₃rc₂rc₁rc₀**
- Always starts with **0100**
- **ra₃ra₂ra₁ra₀** is a 4-bit Register File address (source for A)
- **rb₃rb₂rb₁rb₀** is a 4-bit Register File address (source for B)
- **rc₃rc₂rc₁rc₀** is a 4-bit Register File address (destination)
- Subtracts the 16 bits of B from the 16 bits of A, stores the result in C (all these in the Register File)
- Example: 0100 0001 0010 0011b (or 0x4123) subtracts the data at Register File 2 from the data at Register File 1 and stores the result in Register File 3.

SUBTRACT Instruction

- 0101 0000 00000000
- Always starts 0101 and remainder is all 0s
- Actually is 0100 xxxx xxxxxxxx, since all the bits following 0101 are ignored
- Causes the processor to just stop (**hard stop**)
- You need to reload it or reset it to get it going again.
- Does not involve the Datapath

HALT Instruction

- Sample program:

0: RF[0] = D[0]

1: RF[1] = D[1]

2: RF[2] = RF[0] + RF[1]

3: D[9] = RF[2]

4: HALT

- Becomes:

LOAD 0 0

LOAD 1 1

ADD 0 1 2

STORE 2 9

HALT


This is what gets
stored in Instruction
Memory



0x2000
0x2011
0x3012
0x1209
0x5000

or 0010 00000000 0000b
or 0010 00000001 0001b
or 0011 0000 0001 0010b
or 0001 0010 00001001b
or 0101 0000 00000000b

First Program

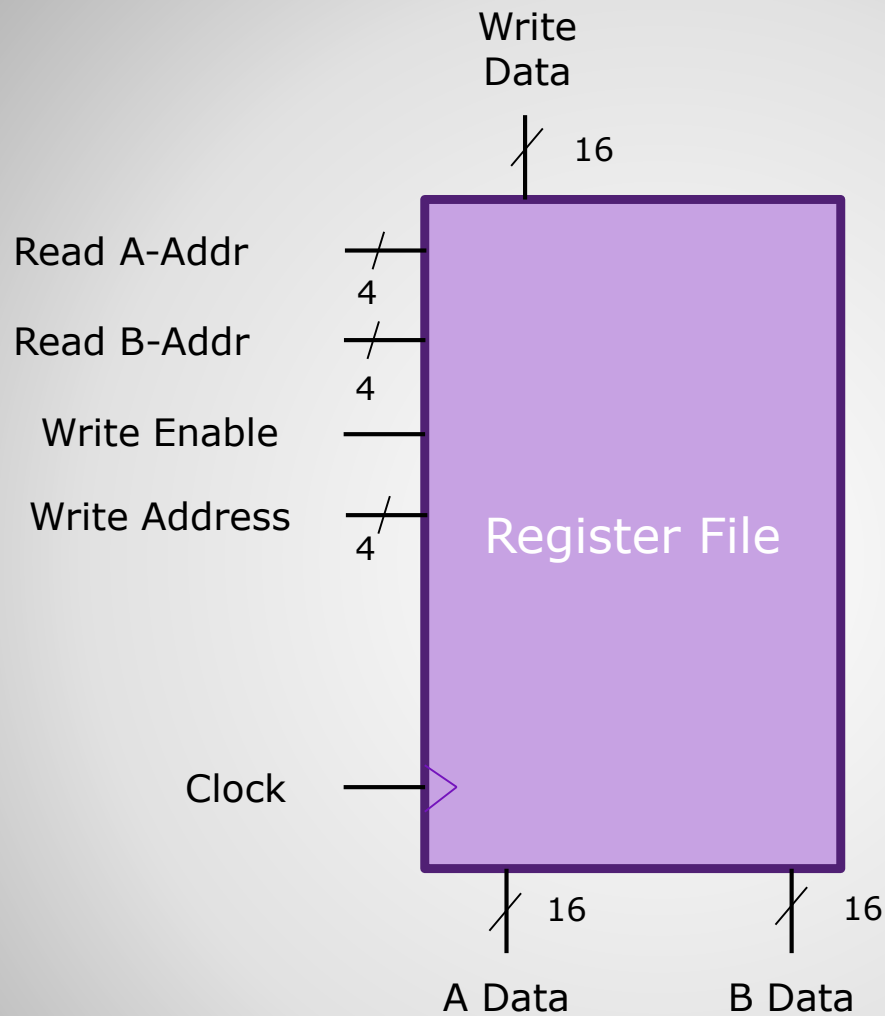

The Register File

```
// This is a Verilog description for an 8 x 16 register file
module regfile8x16a
    (input clk,                // system clock
     input write,              // write enable
     input [2:0] wrAddr,       // write address
     input [15:0] wrData,      // write data
     input [2:0] rdAddrA,      // A-side read address
     output [15:0] rdDataA,    // A-side read data
     input [2:0] rdAddrB,      // B-side read address
     output [15:0] rdDataB ); // B-side read data

    logic [15:0] regfile [0:7]; // the registers

    // read the registers
    assign rdDataA = regfile[rdAddrA];
    assign rdDataB = regfile[rdAddrB];

    always @(posedge clk) begin
        if (write) regfile[wrAddr] <= wrData;
    end
endmodule
```

Expand on this idea for Project B


Suggested Register File Idea

```
// This ALU has eight functions:
//   if s == 0 the output is 0
//   if s == 1 the output is A + B
//   if s == 2 the output is A - B
//   if s == 3 the output is A (pass-through)
//   if s == 4 the output is A ^ B
//   if s == 5 the output is A | B
//   if s == 6 the output is A & B
//   if s == 7 the output is A + 1;
// if additional functions added for future expansion
// you need to expand the selecting signal too
```

Alu_s0 (function select)

3


Datapath

 

```
module ALU( A, B, Sel, Q );
  input [2:0] Sel;      // function select
  input [15:0] A, B;    // input data

  output [15:0] Q; // ALU output (result)
  ...
```

The ALU


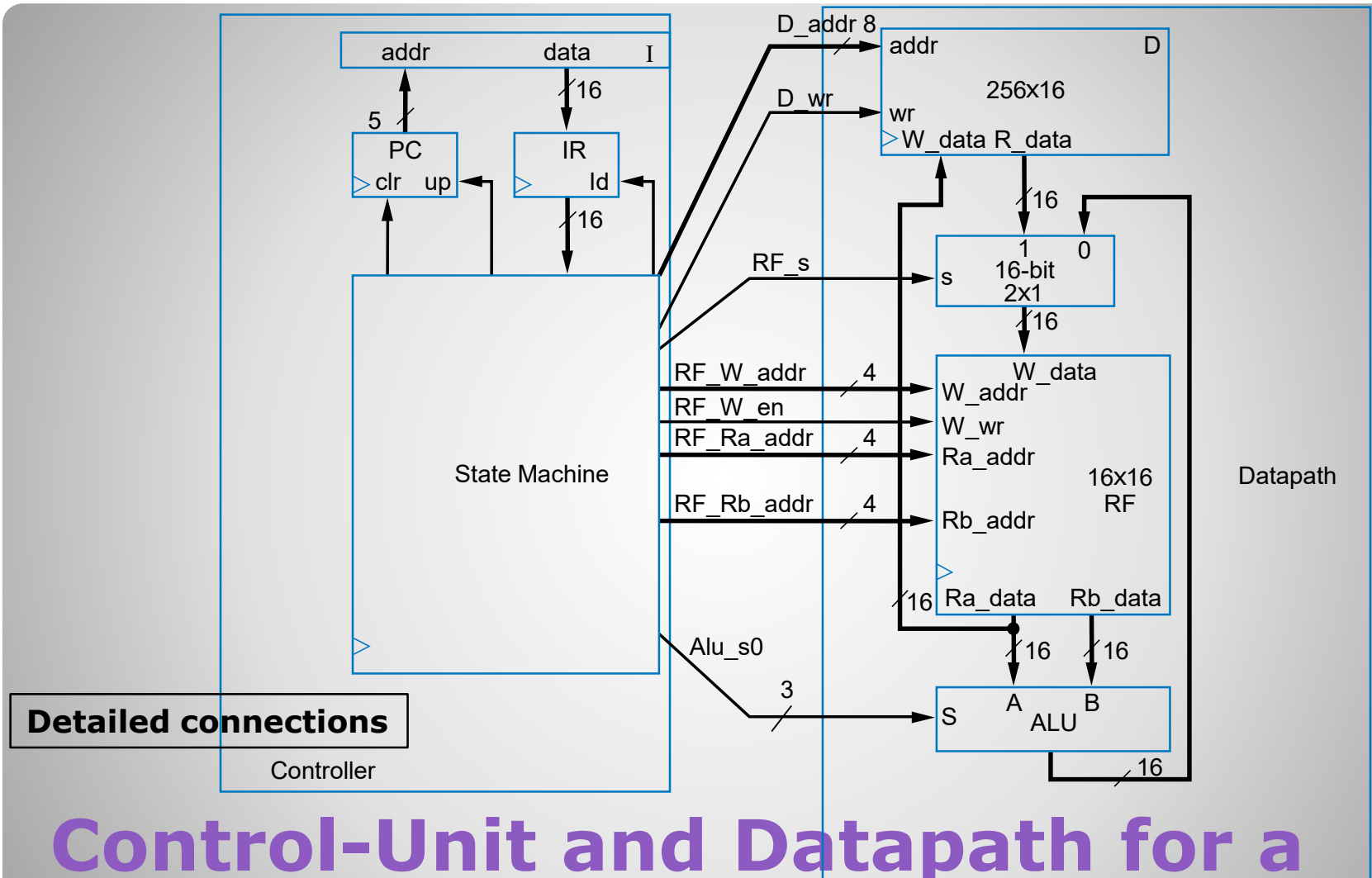


Detailed connections

Controller

Datapath

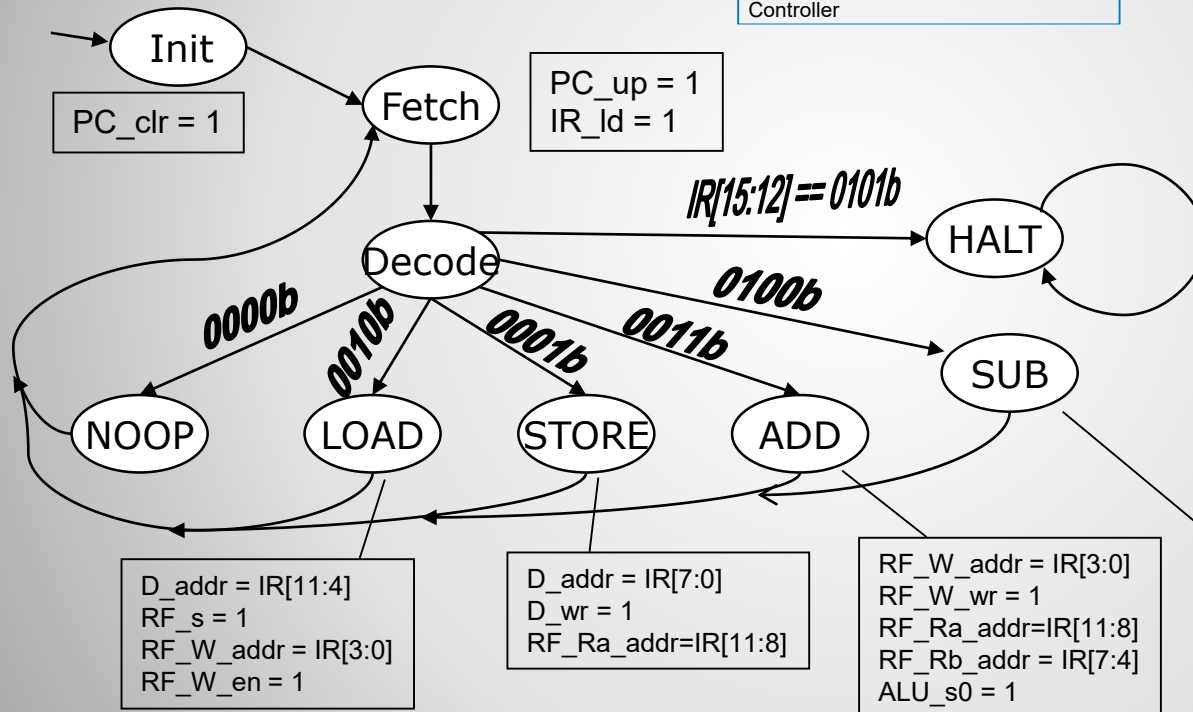 Control-Unit and Datapath for a Programmable Processor (you need some change for ProjectB)



Control Lines

Control	Size
PC_clr	1
PC_up	1
IR_Id	1
D_addr	8
D_wr	1
RF_s	1
RF_W_addr	4
RF_W_en	1
RF_Ra_addr	4
RF_Rb_addr	4
Alu_s0	3

Controller State Machine

State Machine Output Definitions


Variable	Meaning
PC_clr	Program counter (PC) clear command
PC_ld	PC register load command
PC_inc	PC increment command
D_addr	Data memory address (8 bits)
D_wr	Data memory write enable
RF_s	Mux select line
RF_Ra_addr	Register file A-side read address (4 bits)
RF_Rb_addr	Register file B-side read address (4 bits)
RF_Wen	Register file write enable
RF_W_Addr	Register file write address (4 bits)
ALU_s	ALU function select (3 bits)

State Machine State Outputs

State	Non-Zero Outputs
Init	PC_clr = 1
Fetch	IR_ld = 1
Decode	PC_inc = 1
Load	D_addr = IR[11:4], RF_s = 1, RF_A_addr = IR[3:0], RF_Wen = 1
Store	D_addr = IR[7:0], D_wr = 1, RF_A_addr = IR[11:8]
Add, Sub	RF_A_addr = IR[11:8], RF_B_addr = IR[7:4], RFWAddr = IR[3:0], RF_Wen = 1, ALU_s = alu function (1 for Add or 2 for Sub), RF_s = 0
Halt	

- It is recommended to use the combinational loop/sequential loop version.
- Give all your states names using localparams or enums.
- Initialize all outputs to zero at the top of the combinational loop (so that each state has to set only non-zero outputs).
- Set the non-zero outputs in the appropriate state case.
- Sequential part should just check for reset and set state = next state (that's all).

State Machine Considerations

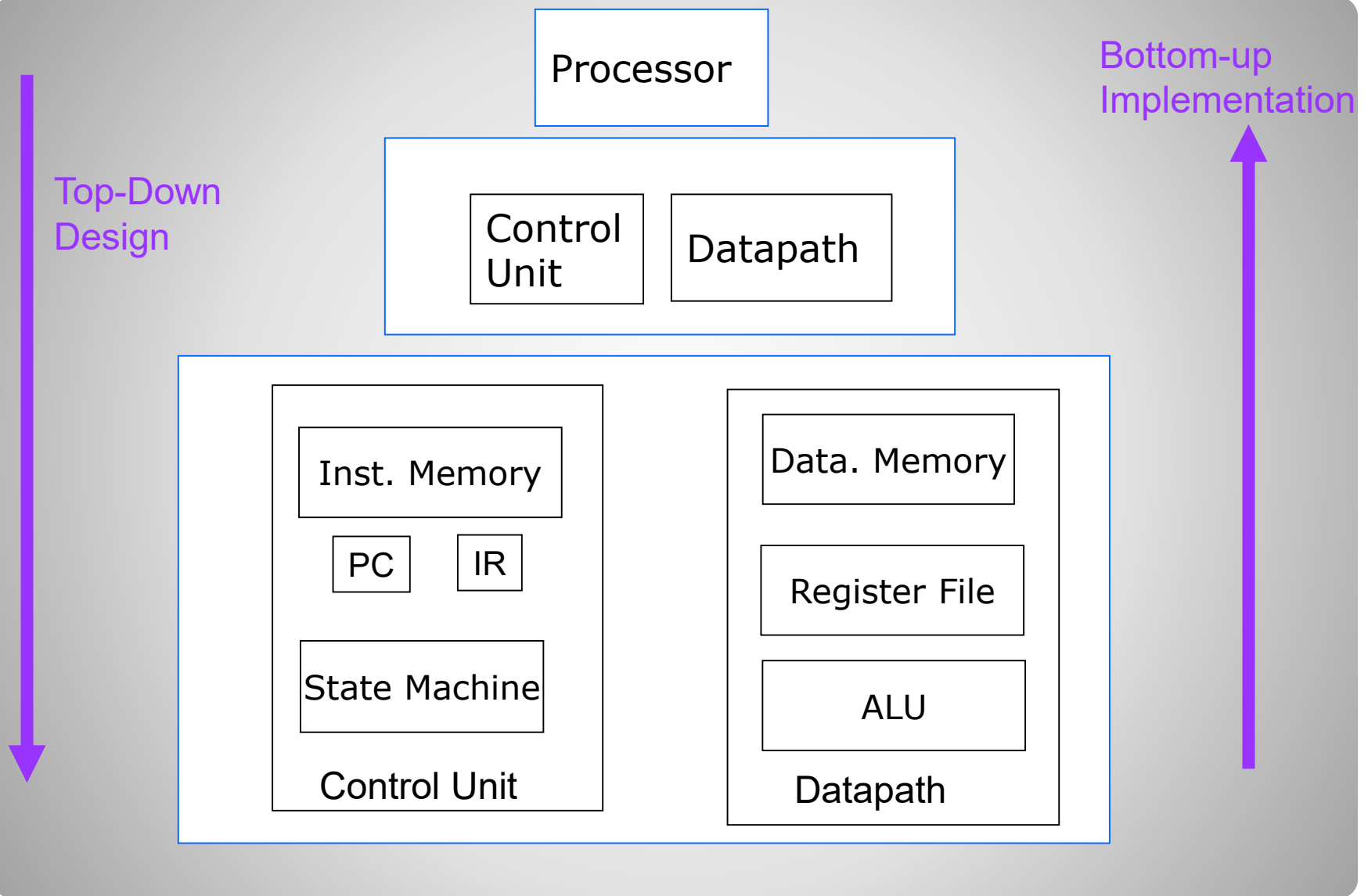

Processor Module Layout

- Write a module (lowest level).
- TEST IT!
- Repeat until you have written all low-level modules.
- Is your state machine recognized as such by Quartus?
- Write the modules next level up (Control Unit, Datapath).
- TEST THESE!
- Write the Processor by instantiating Control Unit module and Datapath module and wiring them together.
- At this point you should be able to test your entire processor in ModelSim.
- Final test for the Processor is running the program and inspecting Data Memory to make sure the correct value is stored there in the correct location.
- NOTE: You can do your unit testing on the DE2 or you can use ModelSim – It's probably better to test with ModelSim because you can more easily debug in this environment.

Procedure